

Exercise Section I (DC circuits analysis)

- For the circuit of Fig.1 find the currents, in microamperes, if the powers absorbed are :
 $P_1 = 27.75 \text{ nW}$, $P_2 = -0.3 \text{ } \mu\text{W}$, and $P_3 = 1.20 \text{ } \mu\text{W}$.

Ans. 18.5, -200, 800

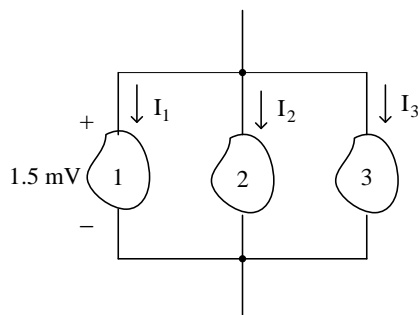


Fig.1

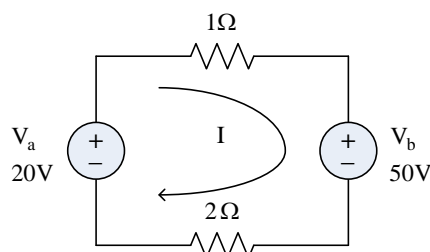


Fig.2

- Find the power delivered by the sources in the circuit of Fig.2

Ans. $P_a = 200 \text{ W}$, $P_b = -500 \text{ W}$

- Find voltages V_1 , V_2 , and V_3 in Fig.3, given that the generalized circuit elements have absorbed powers $P_1 = 250 \text{ W}$, $P_2 = -125 \text{ W}$, and $P_3 = 100 \text{ W}$

Ans. 50 V, -25 V, -20 V

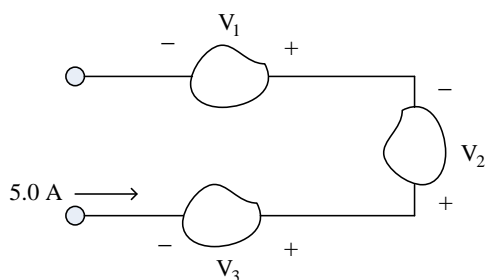


Fig.3

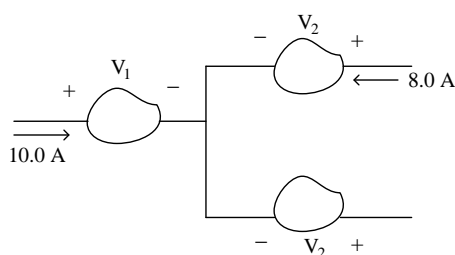


Fig.4

- In the circuit shown in fig.4, $V_1 = 20 \text{ V}$ and $V_2 = V_3 = 15 \text{ V}$. What is the total power absorbed in the three circuit elements ?

Ans. 50 W

- Three resistors are in series and have a total constant voltage V_T . R_1 has a voltage of 20 V, R_2 has a power of 25 W, and $R_3 = 2 \text{ } \Omega$. If the constant current is 5 A, find V_T

Ans. 35 V

- In the circuit shown Fig.5, find the power absorbed by the 5 V battery.

Ans. -5 W

- For the ladder network shown in Fig.6, find the source voltage V_s which results in a current of 7.5 mA in the 3 - Ω resistor.

Ans. 0.705 V

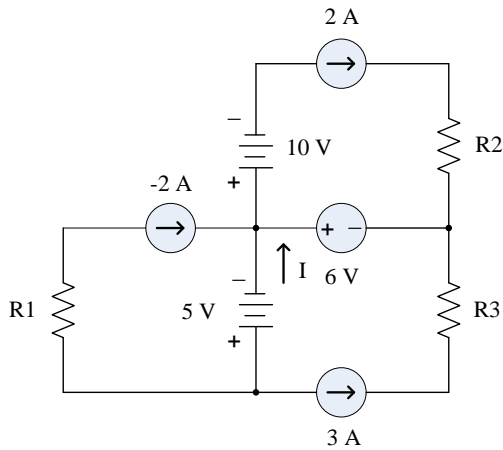


Fig.5

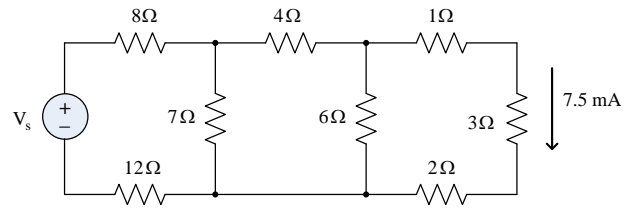


Fig.6

8. The network shown in Fig. 7, obtain the currents in all the network branches.

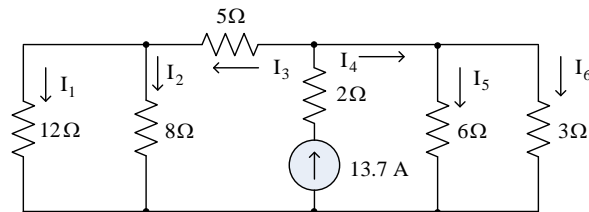


Fig.7

Ans. 0.93, 1.39, 2.32, 11.38, 3.79, 7.59 A

9. Obtain the current in each resistor in Fig. 8 , using network reduction methods.

Ans. $I_A = 1.67$, $I_B = 3.33$, $I_C = 2.50$, $I_D = 1.25$, $I_E = 1.25$, $I_F = 2.50$ A

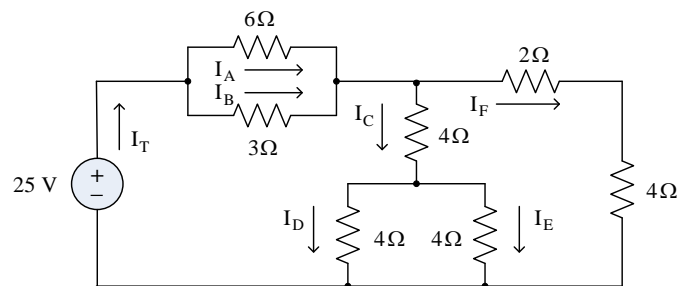


Fig.8

10. Obtain the current I_x in the 10-Ω resistor in Fig.9, using superposition.

Ans. -1 A.

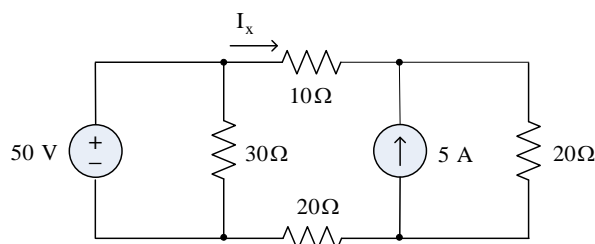


Fig.9

11. Replace the active network to the left of terminal AB in Fig.10 by a thevenin equivalent.

Ans. $R_{TH} = 50 \Omega$, $V_{TH} = 80 \text{ V}$

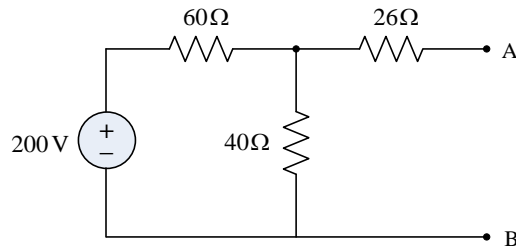


Fig.10

12. Obtain the Norton equivalent for the active network of Problem 11.

Ans. $R_{TH} = 50 \Omega$, $I_N = 1.60 \text{ A}$

13. For the network shown in Fig.11, obtain the mesh currents I_1 , I_2 and I_3

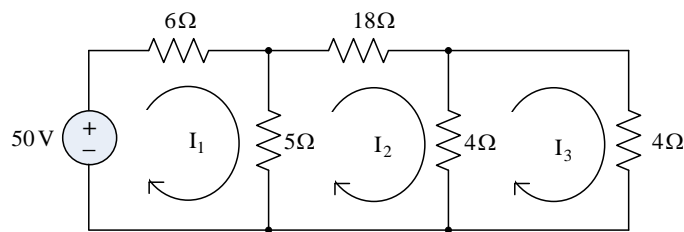


Fig.11

Ans. 5.0, 1.0, 0.5 A

14. Loop currents are shown in the network of Fig.12. Write the matrix equation and solve for I_1 , I_2 and I_3

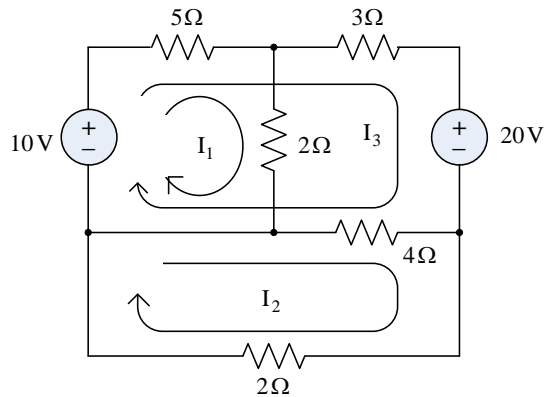


Fig.12

Ans. 3.55, -1.98, -2.98 A

15. The network of Problem 14 has been redrawn in Fig.13 for solution by the node voltage method. Find the node voltages V_1 and V_2 , and with then verify the three currents obtained in Problem 14.

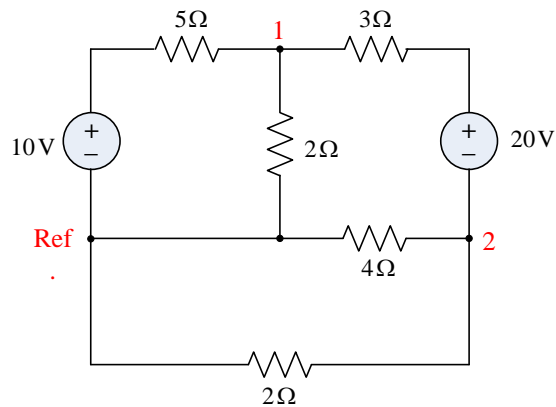


Fig.13

Ans. 7.11, -3.96 V

16. Obtain the four mesh currents in Fig.14

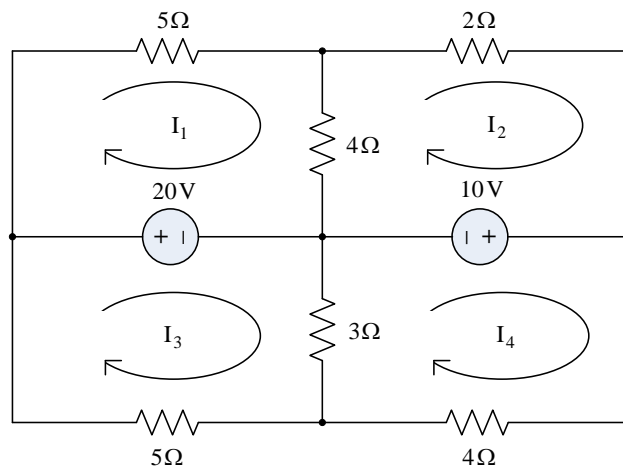


Fig.14

Ans. 2.11, -0.263, -0.34, 0.426 A

17. Find the node voltages V_1 , V_2 , V_3 , and V_4

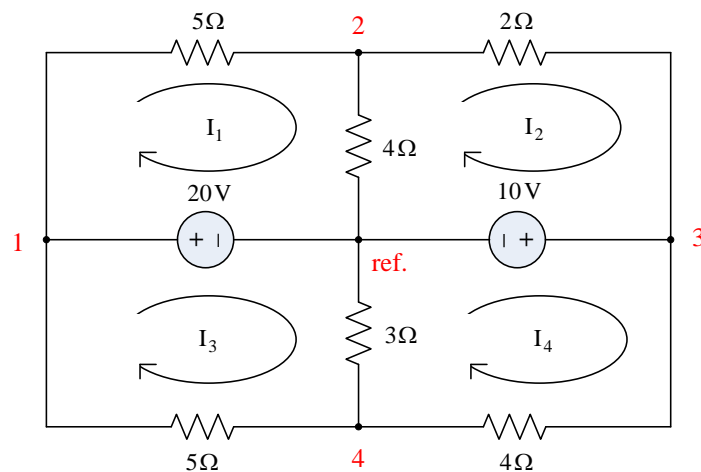


Fig.15

Ans. 20, 9.47, 10, 8.30 V