

Exercise Section II (AC circuits analysis)

1. Find the current in an inductance of 5.0 mH, given the voltage across the element,

$$v = 75 \sin(5000t - 45^\circ) \text{ V}$$

Ans. $i = 3.0 \sin(5000t - 135^\circ) \text{ A}$

2. In Fig.1, $i = 2.5 \cos(1.5 \times 10^6 t + 45^\circ) \text{ A}$. Obtain the voltage v .

Ans. $150 \cos(1.5 \times 10^6 t - 45^\circ) \text{ V}$

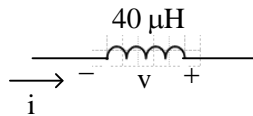


Fig.1

3. The circuit element in Fig.2 has a current $i = 2.5 \cos(2500t - 30^\circ) \text{ A}$ and a voltage $v = 5 \sin(2500t - 30^\circ) \text{ V}$. What is the element ?

Ans. $200 \mu\text{F}$ capacitor

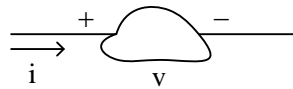


Fig.2

4. The voltage and current sine waves in Fig.3 both pass through zero every 1.26 ms, and the maximum values are 120 V and 0.40 A. What single circuit element does this indicate ?

Ans. a 120 mH inductor

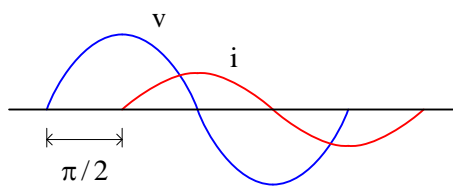


Fig.3

5. Two circuit elements in a series connection have current and total voltage

$$i = 13.42 \sin(500t - 53.4^\circ) \text{ A} \quad v = 150 \sin(500t + 10^\circ) \text{ V}$$

Identify the two elements. Ans. $R = 5 \Omega$, $L = 20 \text{ mH}$

6. Two circuit elements in a series connection have current and total voltage

$$i = 4.0 \cos(2000t + 13.2^\circ) \text{ A} \quad v = 200 \sin(2000t + 50^\circ) \text{ V}$$

Identify the two elements. Ans. $R = 30 \Omega$, $C = 12.5 \mu\text{F}$

7. The circuit shown in Fig.4 has a current $i = 5.0 \sin 2500t$ mA. Find the maximum values of

- (a) v_R
 (b) v_L
 (c) $v_R + v_L$

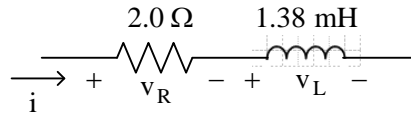


Fig.4

Ans. (a) 10 mV; (b) 17.3 mV; (c) 20 mV

8. A series RC circuit, with $R = 27.5 \Omega$ and $C = 66.7 \mu\text{F}$, has sinusoidal voltage and current, with angular frequency 1500 rad/s. Find the phase angle by which the current leads the voltage.

Ans. 20°

9. A series RLC circuit, with $R = 15 \Omega$, $L = 80$ mH, $C = 30 \mu\text{F}$, has a sinusoidal current at angular frequency 500 rad/s. determine the phase angle and whether the current leads or lags the total voltage.

Ans. 60.6° , leads

10. In Fig.5, $i = 12.5 \cos(3000t - 55^\circ)$ A and $v = 353.5 \cos(3000t - 10^\circ)$ V. Find R and C

Ans. 20Ω , $33.3 \mu\text{F}$

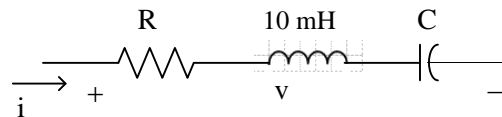


Fig.5

11. A resistance $R = 10 \Omega$ and an inductance $L = 5.0$ mH are in parallel. The inductive – branch current is

$$i_L = 5.0 \sin(2000t - 45^\circ) \text{ A}$$

Obtain the total current, $i_T = i_R + i_L$, and the angle by which i_T lags the voltage v .

Ans. $7.07 \sin(2000t) \text{ A}$, 45°

12. A two – branch parallel circuit, with $R = 10 \Omega$ in one branch and $C = 100 \mu\text{F}$ in the other, has a voltage

$$v = 150 \cos(5000t - 30^\circ) \text{ V}$$

Find the total current, $i_T = i_R + i_C$

Ans. $76.5 \cos(5000t + 48.7^\circ) \text{ A}$

13. A capacitor $C = 35 \mu\text{F}$ is in parallel with a certain element. Identify the element, given that the voltage and total current are

$$v = 150 \sin 2000t \text{ V} \quad i_T = 16.5 \sin(3000t + 72.4^\circ) \text{ A}$$

Ans. $R = 30.1 \Omega$

14. three parallel branches respectively contain $R = 300 \Omega$, $L = 0.50 \text{ H}$, $C = 10 \mu\text{F}$. Given the voltage $v = 200 \sin 1000t \text{ V}$, determine if the total current leads or lags the voltage, and by how much.

Ans. Leads by 67.4°

15. Use phasor methods to obtain the current i in Fig.6 , given

$$i = 14.14 \cos(800t - 45^\circ) \text{ A}$$

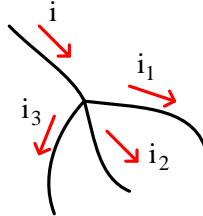


Fig.6

Ans. $32.4 \cos(800t + 8.9^\circ) \text{ A}$

16. Use phasor methods to obtain the current v_1 in Fig.7 , given

$$v_2 = 50 \sin(\omega t + 63.4^\circ) \text{ V} \quad v = 67.1 \cos(\omega t - 8.48^\circ) \text{ V}$$

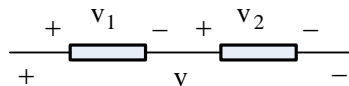


Fig.7

Ans. $25 \cos(800t + 30^\circ) \text{ V}$

17. For the circuit shown in Fig.8 , obtain Z_{eq} and compute I

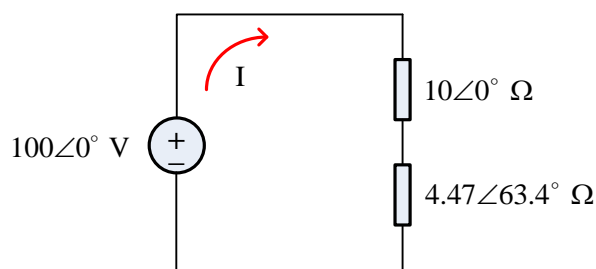


Fig.8

Ans. $7.91 \angle -18.43^\circ \text{ A}$

18. Evaluate the impedance Z_1 in the circuit of Fig.9

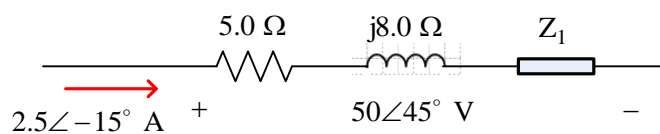


Fig.9

Ans. $5.0 + j9.3 \Omega$

19. Compute the equivalent impedance Z_{eq} and admittance Y_{eq} for the four-branch circuit of Fig.10

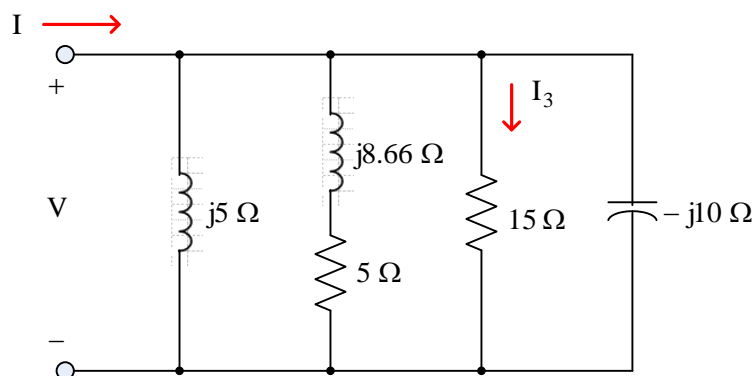


Fig.10

Ans. $Z_{eq} = 4.53 \angle 58^\circ \Omega$, $Y_{eq} = 0.22 \angle -58^\circ S$

20. The total current I entering the circuit shown in Fig.10 is $33 \angle 13^\circ A$. Obtain the branch current I_3 and the voltage V .

ans. $I_3 = 9.97 \angle 45^\circ A$, $V = 149.5 \angle 45^\circ V$

21. Find I_1 and I_2 in the parallel circuit of Fig.11

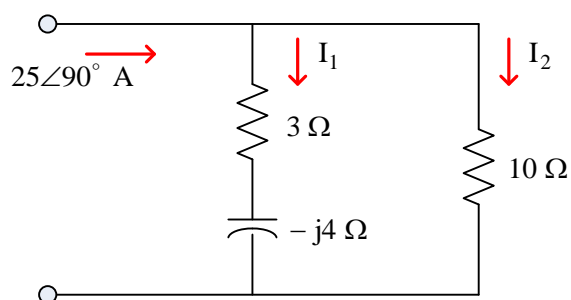


Fig.11

Ans. $I_1 = 18.4 \angle 107.1^\circ A$, $I_2 = 9.19 \angle 54^\circ A$,

22. For the network of Fig.12 . Obtain I_1 , I_2 , I_3

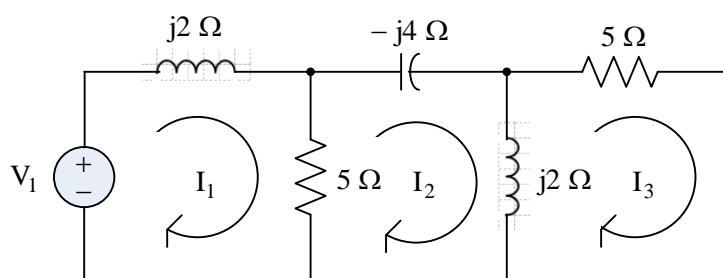


Fig.12

23. Using the node voltage method, find the voltage of node 1 in Fig.13 with respect to the reference.

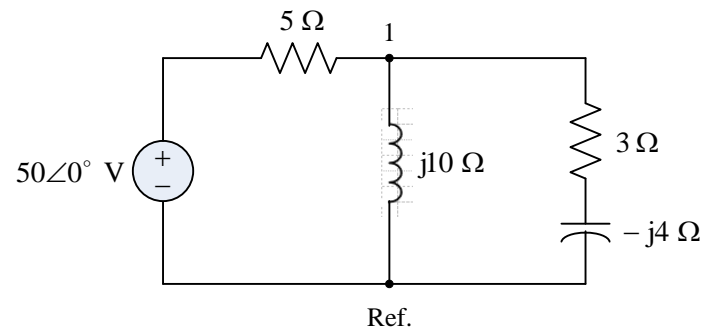


Fig.13

Ans. $30.7\angle -10.6^\circ \text{ V}$